

--	--	--	--	--	--	--	--

(For those admitted in June 2023 and later)

SEM	CATEGORY	COMPONENT	COURSE CODE	COURSE TITLE
II	PART-III	CORE-3	U23EL202	DIGITAL ELECTRONICS

Maximum: 75 Marks

1

Course Outcome	Bloom's K-level	Q. No.	<p align="center">SECTION – B (5 X 5 = 25 Marks) Answer <u>ALL</u> Questions choosing either (a) or (b)</p>
CO1	K3	11a.	Show the binary addition $(-43) + (-78)$. (OR)
CO1	K3	11b.	Illustrate the ASCII code with an example.
CO2	K3	12a.	Simplify the expression $Y = \sum_m (7, 9, 11, 12, 13, 14, 15)$, using the K-map method.
CO2	K3	12b.	(OR) Explain the function of AND gate with neat diagram.
CO3	K4	13a.	Describe the working of a full-adder with neat logic circuit. (OR)
CO3	K4	13b.	Design a 1-to-4 demultiplexer and explain its operation.
CO4	K4	14a.	Describe the 4 bit serial-in-serial out shift register with neat logic diagram (OR)
CO4	K4	14b.	Compare shift register with counter.
CO5	K5	15a.	Explain the difference between RAM and ROM. (OR)
CO5	K5	15b.	Discuss the function of programmable array logic.

Course Outcome	Bloom's K-level	Q. No.	<p align="center">SECTION – C (5 X 8 = 40 Marks) Answer <u>ALL</u> Questions choosing either (a) or (b)</p>
CO1	K3	16a.	Perform the following conversion (i). $(A6F)_{16} = \text{-----} ()_8?$ (ii). $(127)_{10} = \text{-----} ()_2?$ (iii). $(3764)_8 = \text{-----} ()_{16}?$ (iv). $(11101)_2 = \text{-----} ()_{10}?$ (OR)
CO1	K3	16b.	Briefly explain the Excess-3 code, Gray code.
CO2	K4	17a.	State Boolean laws and theorems. (OR)
CO2	K4	17b.	Explain how the basic gates can be realized using NOR and NAND gates.
CO3	K4	18a.	Show how a full adder can be converted to a full-subtractor with the addition of an inverter circuit.
CO3	K4	18b.	(OR) Illustrate the binary to gray and gray to binary code converter logic circuit.
CO4	K5	19a.	Explain the operation of J-K flip-flop and master-slave J-K flip-flop. (OR)
CO4	K5	19b.	Explain the working of 4-bit ring counter with neat logic circuit.
CO5	K5	20a.	Classify the different types of ROM and explain in detail. (OR)
CO5	K5	20b.	Discuss in detail about field programmable gate arrays.