

--	--	--	--	--	--	--	--

G. VENKATASWAMY NAIDU COLLEGE (AUTONOMOUS), KOVILPATTI – 628 502.



UG DEGREE END SEMESTER EXAMINATIONS - NOVEMBER 2025.

(For those admitted in June 2023 and later)

PROGRAMME AND BRANCH: B.C.A.

SEM	CATEGORY	COMPONENT	COURSE CODE	COURSE TITLE
IV	PART-III	ELECTIVE GENERIC-4	U23CA4A4	DIGITAL LOGIC FUNDAMENTALS

Date & Session: 07.11.2025/FN

Time: 3 hours

Maximum: 75 Marks

Course Outcome	Bloom's K-level	Q. No.	SECTION – A (10 X 1 = 10 Marks) Answer <u>ALL</u> Questions.
CO1	K1	1.	Which of the following is a universal logic gate? a) AND b) OR c) NOR d) NOT
CO1	K2	2.	Which Boolean law states: $A + 0 = A$? a) Identity Law b) Complement Law c) Domination Law d) Idempotent Law
CO2	K1	3.	What is the binary equivalent of the decimal number 37? a) 100101 b) 101001 c) 110101 d) 100011
CO2	K2	4.	The Don't Care conditions in a Karnaugh Map are used to a) Make the Boolean expression more complex b) Represent undefined or unused combinations c) Increase the number of variables d) Represent binary values
CO3	K1	5.	What is the base of the hexadecimal number system? a) 8 b) 16 c) 10 d) 2
CO3	K2	6.	How is a Boolean function represented in the Product-of-Sums (POS) form? a) AND of OR terms b) OR of AND terms c) XOR of OR terms d) NOR of AND terms
CO4	K1	7.	Which of the following is a combinational circuit used for binary addition? a) Decoder b) Multiplexer c) Half Adder d) Flip-Flop
CO4	K2	8.	What is the sum of $(1011)_2 + (1101)_2$ in binary? a) 10100 b) 11000 c) 11100 d) 10000
CO5	K1	9.	Which component is responsible for performing arithmetic and logic operations in a CPU? a) Control Unit b) Register c) ALU d) Decoder
CO5	K2	10.	In an Adder-Subtractor circuit, what determines whether the circuit performs addition or subtraction? a) Control bit b) Carry bit c) Overflow bit d) Sign bit
Course Outcome	Bloom's K-level	Q. No.	SECTION – B (5 X 5 = 25 Marks) Answer <u>ALL</u> Questions choosing either (a) or (b)
CO1	K3	11a.	Derive the truth table for an Ex-OR gate and its Boolean expression. (OR)
CO1	K3	11b.	Define the significance of Boolean laws and theorems with examples.

